



# (Yet Another) Universal PLL Source for Low VHF Through Microwave

Joe Haas, KEØFF  
Ben Bibb, NO5K

(Or...what I did on my spring vacation)

# Why?

Mkr  $\Delta 100.0\mu S$   
Ref Lvl 10.

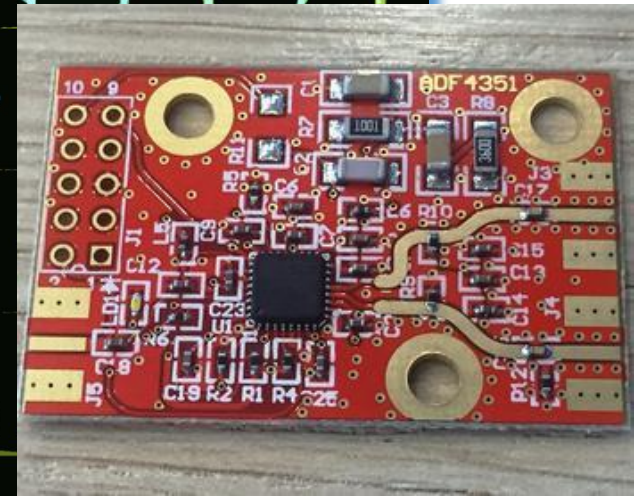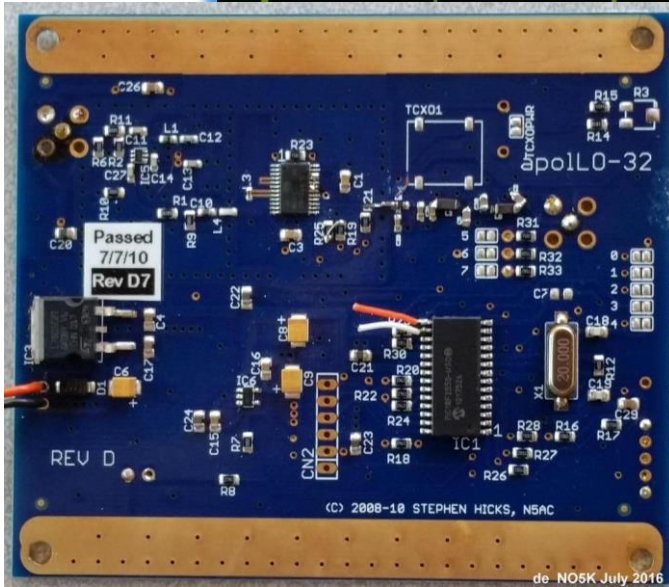

Freq 902.138  
ResBW 30kHz

[LEVEL] [RESBW]

26

an  
SWP 1.0ms



MHz
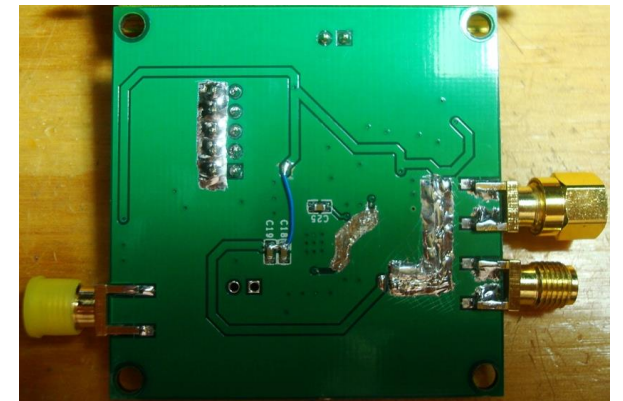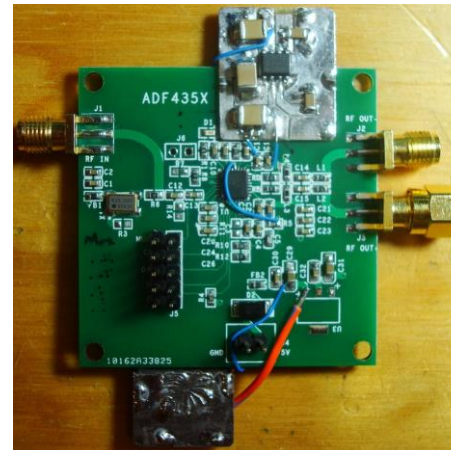
# I'm NOT going to discuss "WHY?" ...

- OK, this is why:




T/G Project: needed a  $\mu\text{W}$   
(3.6214 GHz) source:



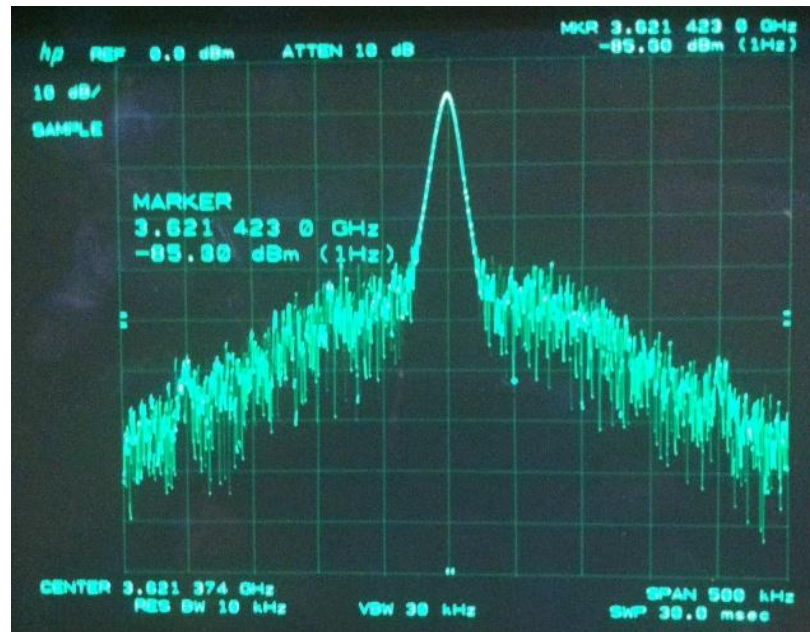
# “Store-Bought” Synthesizer

- Extensive modifications to layout and power supplies



Original output at 3.6 GHz

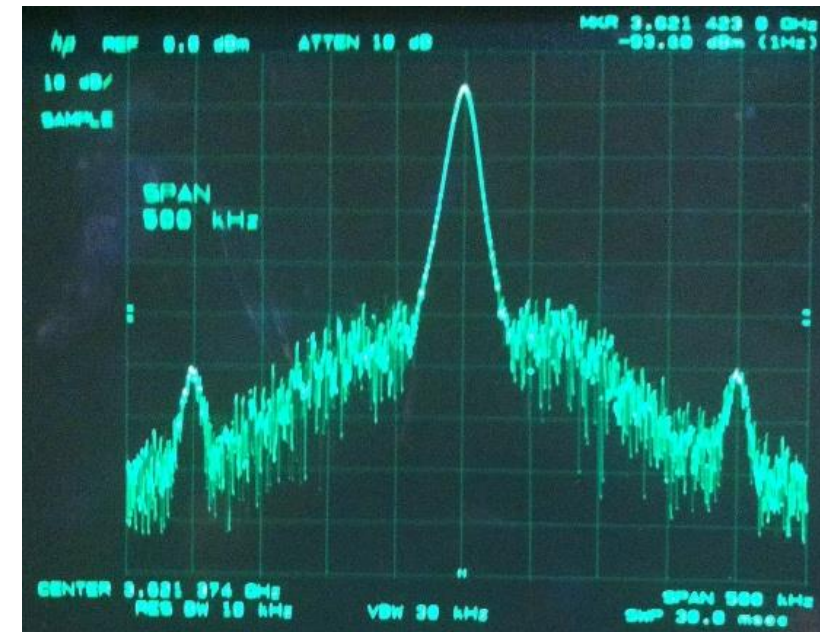

3.6 GHz output after adding  
one ULN-LDO

- Addition of two ULN-LDOs ultimately reduces PN by about 23 dB/Hz

# Soon, other needs arose:


- Signal Generator/Sweep osc.
- Transmitters
- XVRTR LOs
- Beacons
- etc...

Overarching need:

Stand-alone operation (No PC needed to operate).

(THAT's why)

# The Basic PLL

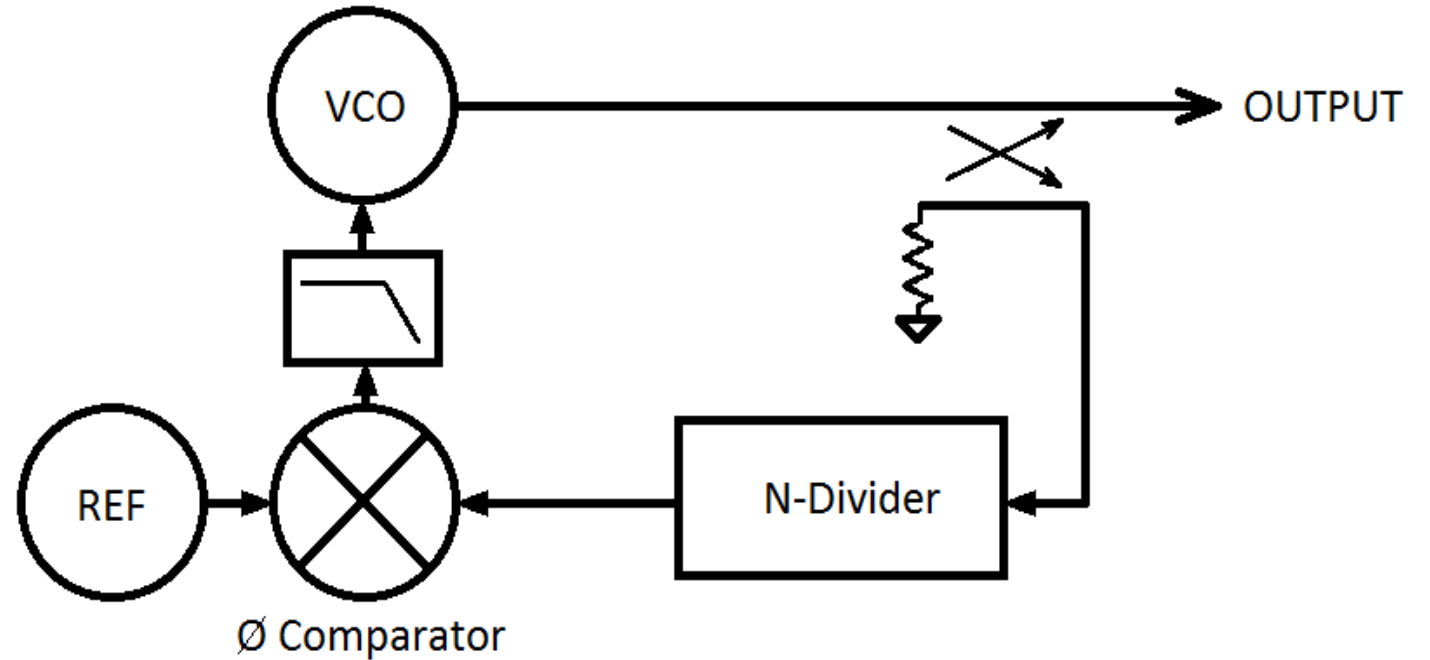


## Basic Components:

- VCO Fc output across a given BW (Fc from Audio to  $\mu\text{W}$ , depending on application)
- Splitter/Coupler (configuration depends on cost and performance requirements)
- N-Divider “reduces” VCO frequency to “match” the REF oscillator
- The phase comparator produces an error signal that feeds the VCO
- The loop filter removes unwanted harmonics and spurious components from the error signal.
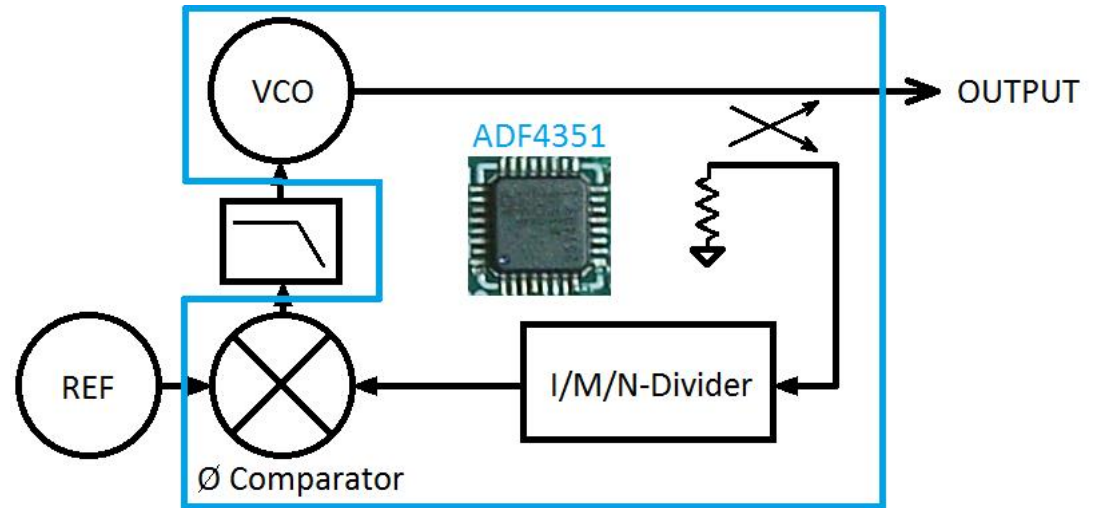
# The ADF-4351 Is the “Whole Enchilada”

- Integrated VCO
- Covers 35 to 4400 MHz
- Small size
- Reasonable cost.
- Fine-frequency resolution
- Requires a controller to program internal configuration registers



All that is needed is a Microcontroller, a decent REF oscillator, and a few passive components (and really quiet power supplies).


# The Pudding

The Orion-I design specifications:


- 100 Channels (8 bits, 2-digit BCD)
- Serial control option (RS-232)
- Field-selectable on-board/ext REF (option)
- +10dBm out
- “Reasonable” PN ( $\sim\sim$  -100 dBc/Hz or better at 1KHz)
- “PTT” input (option)
- Other possibilities: Sweep, Morse ID, etc... (it’s just software, man!)
- Parts cost <\$70 (pedigreed parts, QTY 1) – Mass production can reduce cost considerably




# ADIsimPLL Design SW

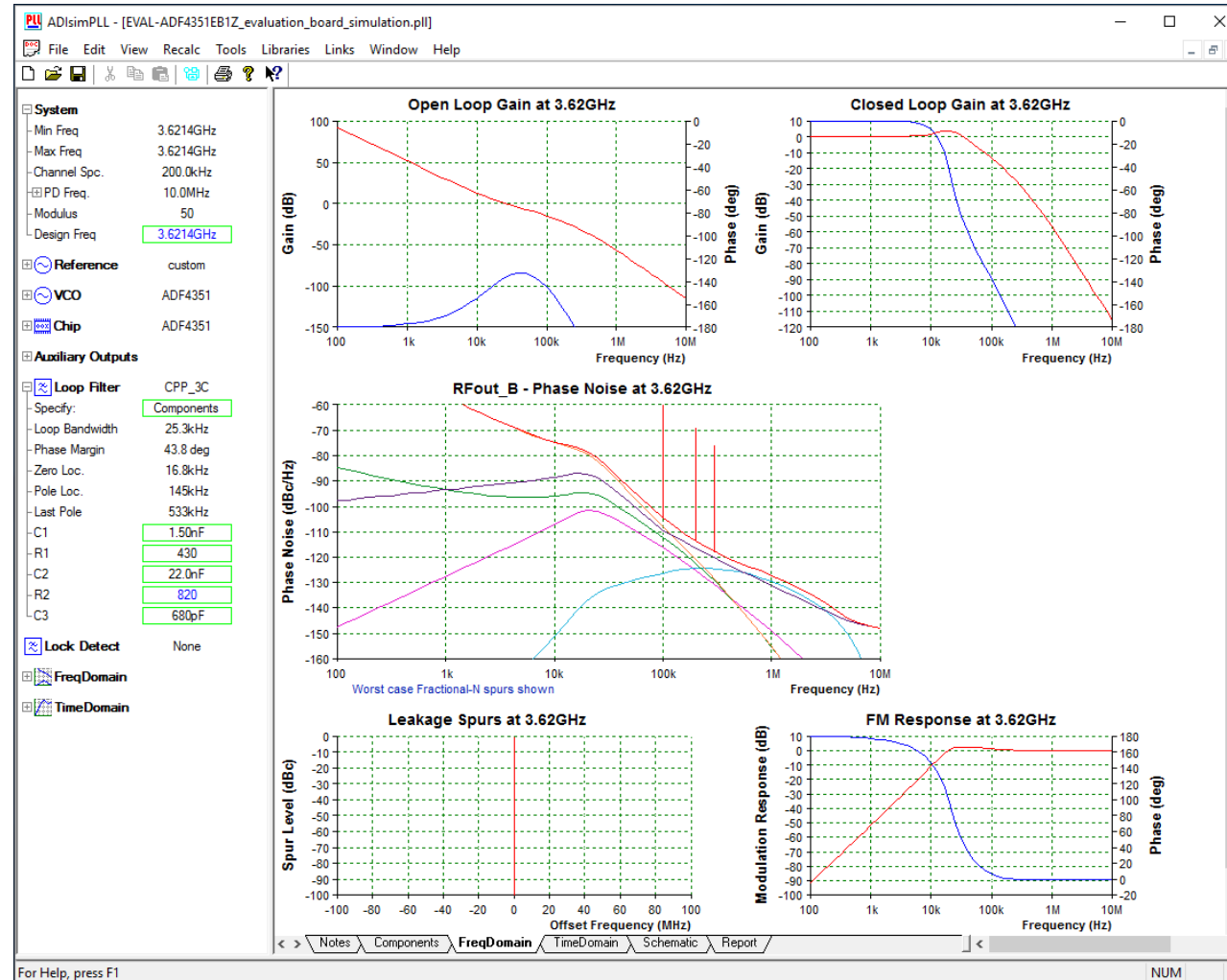



# Simplified Schematic

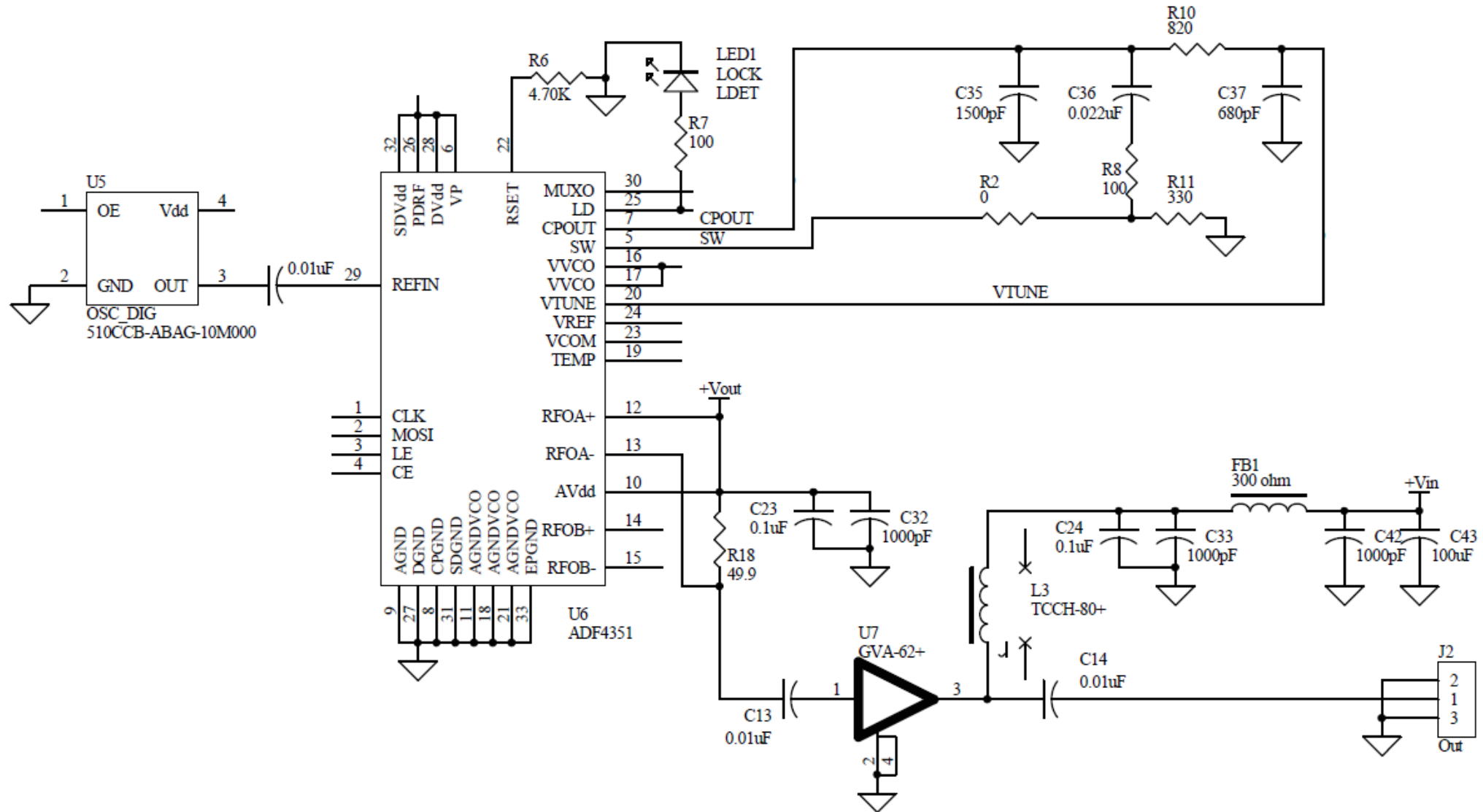


# No Kitchen Sink...

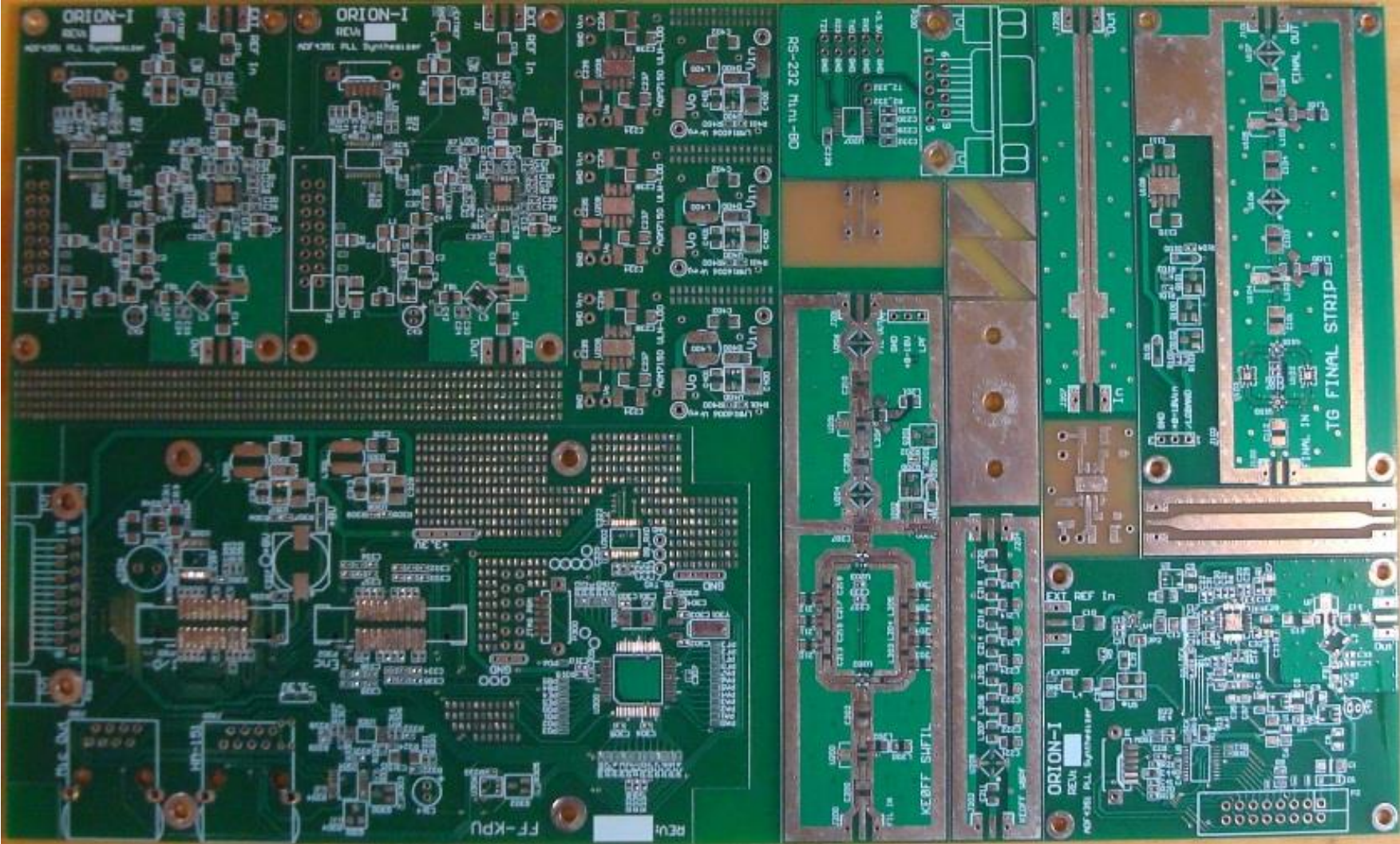

Ta...Da.

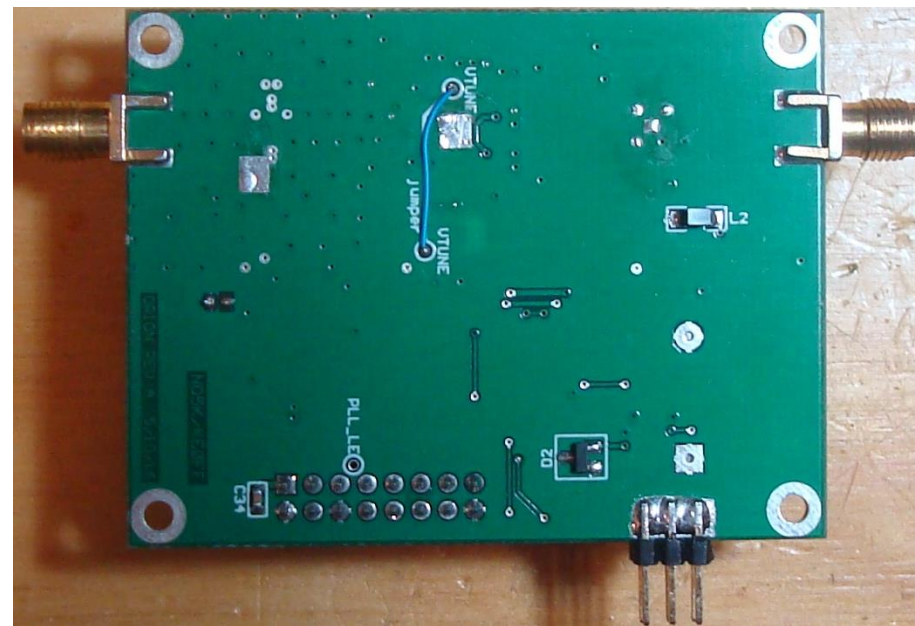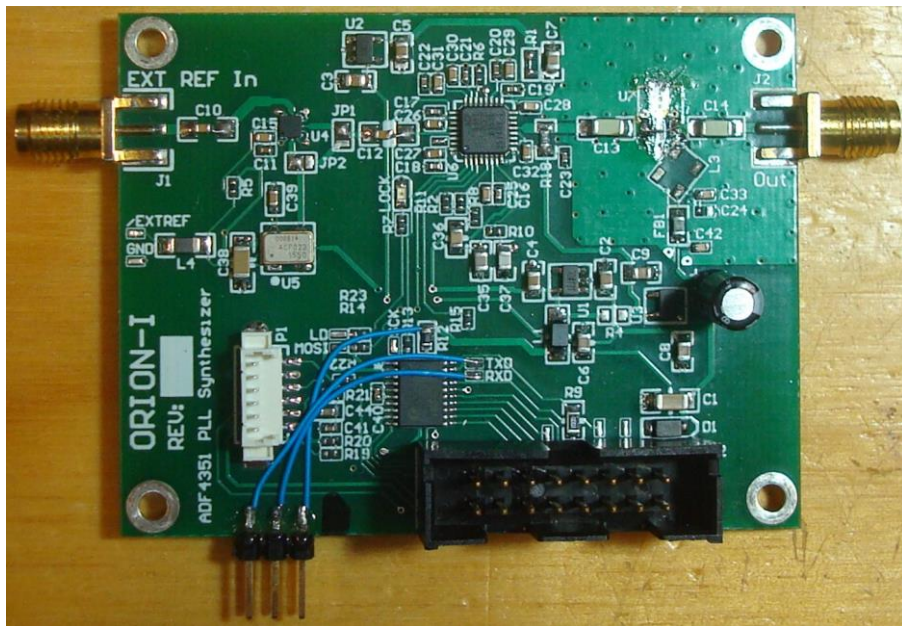


# Plots (PN)

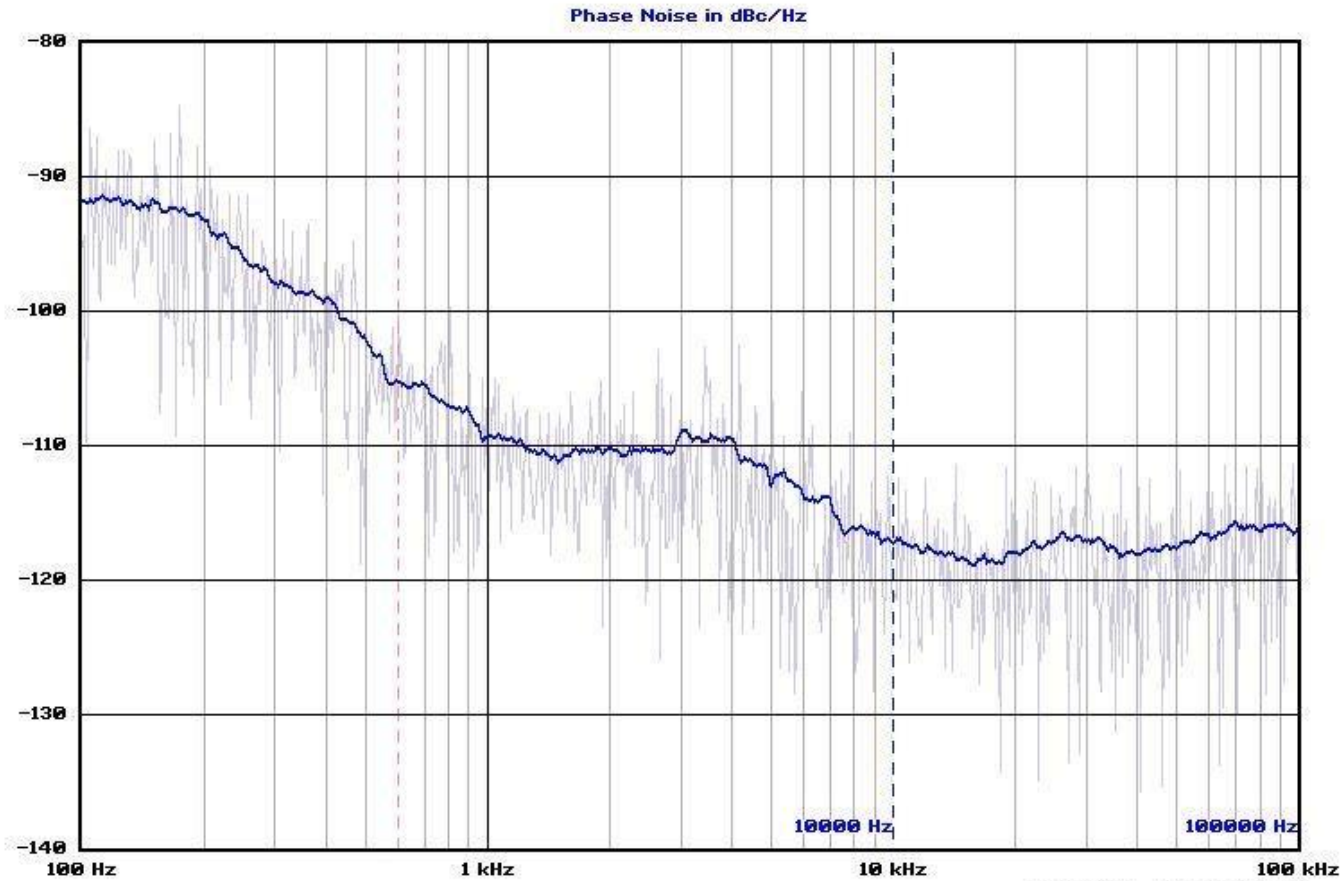

de N05K 03 Aug 2016

Trace	Carrier Hz	dBc/Hz at 600 Hz	Residual FM Hz	RMS Jitter	Instrument
ORION-I S/N 01 at N05K	902 166 900	-105.3	3.90E+001	1.1E-013 s	TEK/2782

# Plots (PLP-1000+ LPF)

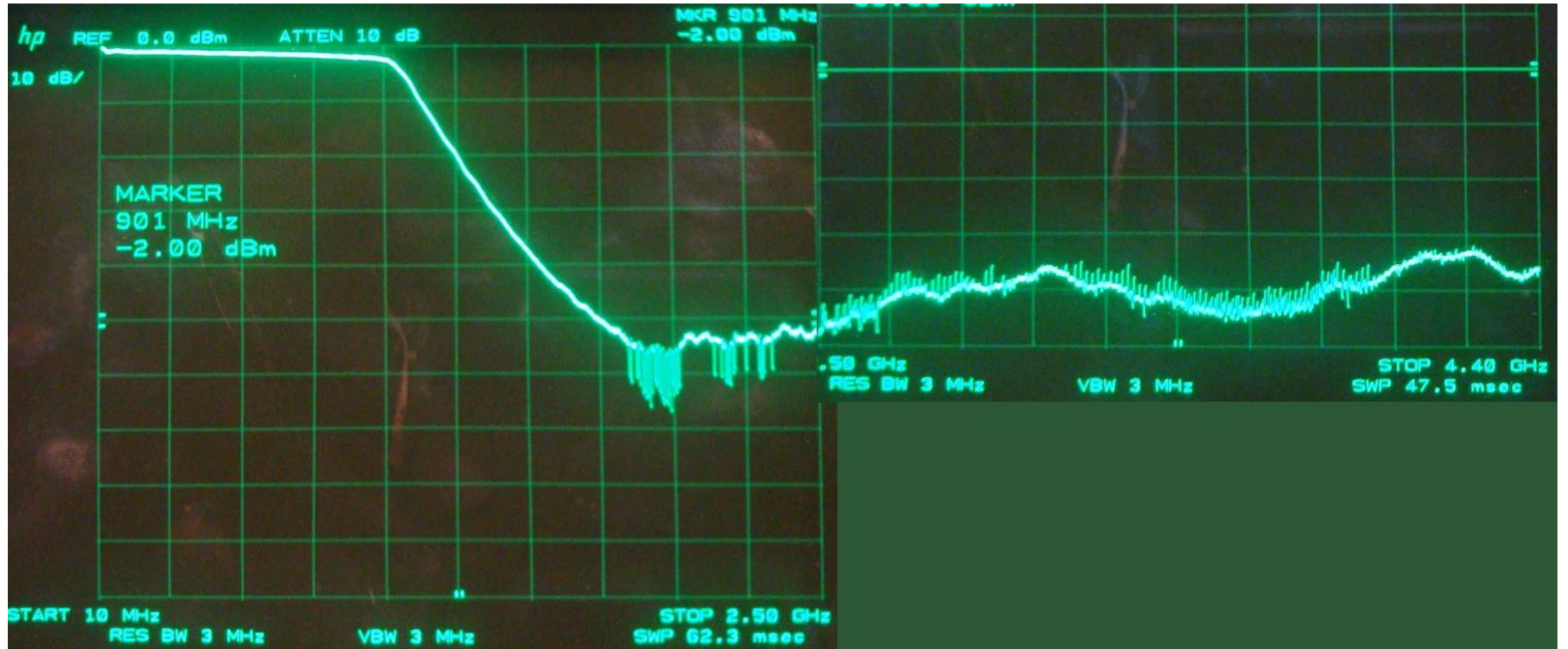


# UX-902

## 902 MHz FM TX module for the IC-901

- Single channel
- Looks like a UX-129 (1200MHz) in the IC-901 stack
- 18W output, max. Dialed back to 4 W (high) and 400mW (low)
- Modulation injected at Vtune pin of the ADF4351
- This injection method requires baseband frequency compensation to counteract PLL response



# FM Test Set

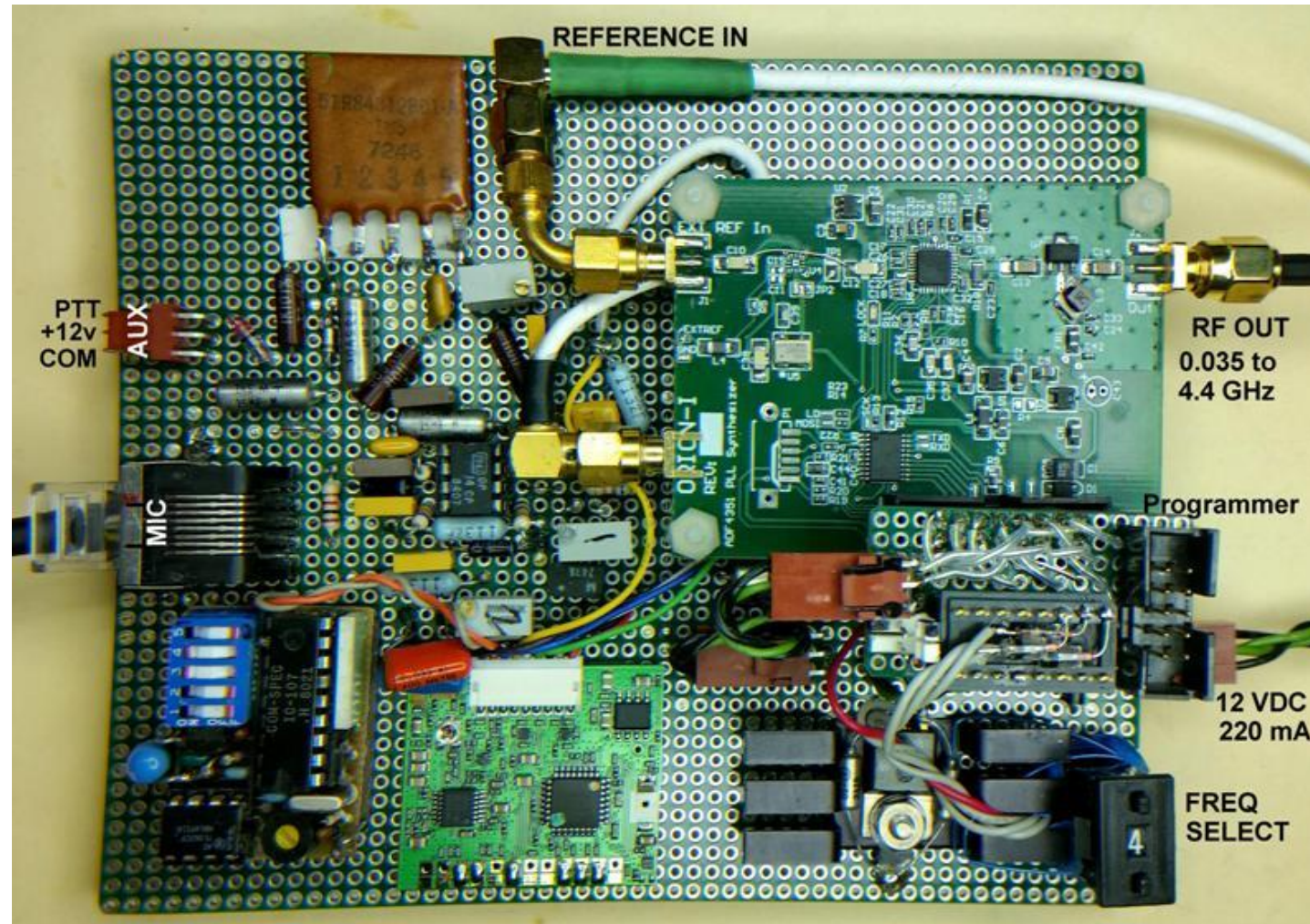



# Links/References

- ADF-4351 Datasheet:
  - <http://www.analog.com/media/en/technical-documentation/data-sheets/ADF4351.pdf>
- ADIsimPLL:
  - [https://form.analog.com/form\\_pages/rfcomms/adisimpll.aspx](https://form.analog.com/form_pages/rfcomms/adisimpll.aspx)
- RMG:
  - <http://www.k5rmg.com/>
- KEØFF Projects:
  - <http://www.rollanet.org/~joeh/projects/>